

LAB02\_312651057

吳鴻明

# 實驗目的

透過RTL coding實現24小時制的電子鐘，熟悉記憶元件D-Flip-Flop，以及如何將50MHZ的Clock降為1HZ，實現1秒步進的時鐘




實驗程式碼

```
time_bg.v X timer.v
time_bg.v
1  /*Original code by <HONG-MING-WU>*/
2  module cclock(CLOCK_50,SW,HEX0,HEX1,HEX2,HEX3,HEX4,HEX5);
3  input CLOCK_50;
4  input [9:0]SW;
5  output reg [6:0]HEX0,HEX1,HEX2,HEX3,HEX4,HEX5;
6
7  //reg declare
8  reg[26:0]sys_cnt; //use to count 1 second
9  reg[5:0]sec_cnt; //use to count real second
10 reg[7:0]min_cnt; //use to count minute
11 reg[7:0]hr_cnt; //use to count hour
12 reg SW8_ff;
13 //wire declare
14 wire SW8_n;
15
16 //delay one cycle
17 always@(posedge CLOCK_50)begin
18     SW8_ff <= SW[8];
19 end
20
21 //
22 always@(posedge CLOCK_50 )begin
23     if ((SW[9]==1'b1)&&(SW8_ff==1'b0)&&(SW[8]==1'b1))begin
24         hr_cnt <= SW[7:0];
25     end
26     else if ((SW[9]==1'b0)&&(SW8_ff==1'b0)&&(SW[8]==1'b1))begin
27         min_cnt <= SW[7:0];
28     end
29     //when sys_cnt reaches 50000000, it means 1 second has passed
30     else if(sys_cnt < 50000000)begin
31         sys_cnt <= sys_cnt+26'b1;
32     end
33
34     else begin
35         sys_cnt <= 0;
36         if ((sec_cnt == 6'd59)&&(min_cnt == 6'd59)&&(hr_cnt == 6'd23))begin
37             sec_cnt <= 0;
38             min_cnt <= 0;
39             hr_cnt <= 0;
40         end
41         else if ((sec_cnt == 6'd59)&&(min_cnt == 6'd59))begin
42             sec_cnt <= 0;
43             min_cnt <= 0;
44             hr_cnt <= hr_cnt+1;
45         end
46         else if ((sec_cnt == 6'd59))begin
47             sec_cnt <= 0;
48             min_cnt <= min_cnt+1;
```

```
time_bg.v X timer.v
time_bg.v
22  always@(posedge CLOCK_50 )begin
34      else begin
45          end
46          else if ((sec_cnt == 6'd59))begin
47              sec_cnt <= 0;
48              min_cnt <= min_cnt+1;
49          end
50          else begin
51              sec_cnt <= sec_cnt+1;
52          end
53      end
54  end
55
56
57  /*The reason why I didn't use this part
58  ,Because I didn't solve the problem of pull down set_valid signal.*/
59
60  /*always@(posedge SW[8])begin
61      if (SW[9]==1'b1)begin
62          set_hr <= SW[7:0];
63          set_valid <= 1'b1;
64      end
65      else if (SW[9]==1'b0)begin
66          set_min <= SW[7:0];
67          set_valid <= 1'b1;
68      end
69  end*/
70
71  //sec display
72  > always@(*)begin ...
359  end
360
361  //min display
362  > always@(*)begin ...
654  end
655
656  //hour diplay
657  > always@(*)begin ...
773  end
774  endmodule
```



實驗結果照片

   



# 問題與討論

討論：針對本次LAB，比上次的難了一點，但還可以接受，主要原因是多了記憶元件，所以衍伸出了很多問題。

問題：左下圖是我在coding時遇到的問題，我如果設定小時與分鐘後，都會把set\_valid設為1，但這就是問題點，如果我設為1，我就無法在always block裡面把他拉下來變0，也有可能是我沒想到，但最後還是換了一個寫法，如實驗程式碼那邊所張貼的。

```
/*The reason why I didn't use this part  
,Because I didn't solve the problem of pull down set_valid signal.*/  
  
/*always@(posedge SW[8])begin  
    if (SW[9]==1'b1)begin  
        set_hr <= SW[7:0];  
        set_valid <= 1'b1;  
    end  
    else if (SW[9]==1'b0)begin  
        set_min <= SW[7:0];  
        set_valid <= 1'b1;  
    end  
end*/
```